

Fourth Semester B.E. Degree Examination, December 2010

Power Electronics

Time: 3 hrs.

Max. Marks:100

- Note: 1. Answer any FIVE full questions, selecting at least TWO questions from each part.
2. Any missing data may be suitably assumed

PART - A

- What are the advantages of static power converters? Mention the peripheral effects of such static power converters. (08 Marks)
 - Mention the various types of power semiconductor devices. Draw the V-I characteristics and symbols of any five types. Mention their important applications. (12 Marks)
- With a neat circuit diagram, explain 'anti-saturation' control of base drive for BJT. (10 Marks)
 - What is the need of isolation between gate /base drive and power terminal of power converter circuits? Explain two methods, with a neat circuit. (10 Marks)
- Using two transistor model, explain how a small gate current can TURN ON a SCR when blocking forward voltage. (12 Marks)
 - Distinguish between holding current and latching current of thyristor. (04 Marks)
 - For the circuit below, Fig. Q3 (c), if the latching current is 4 mA, find the minimum width of gating pulse required to properly TURN ON the SCR. (04 Marks)

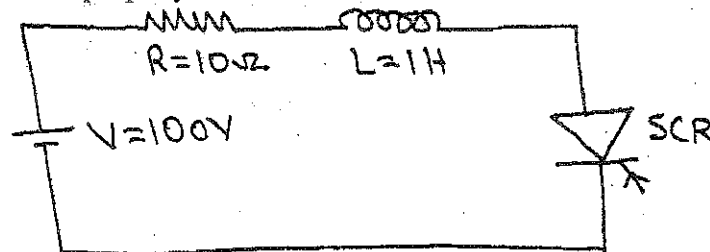


Fig. Q3(c)

- Distinguish between natural and forced commutation and mention the application. (04 Marks)
 - With the help of circuit diagram and relevant waveforms, explain the working of resonant pulse commutation. (10 Marks)
 - Circuit of Fig.4(c) illustrates class D commutation. For this circuit $V_S = 230 V$, $L = 20 \mu H$ and $C = 40 \mu f$. for a constant load current of 120A, calculate peak value of current through capacitance and also through main and auxiliary thyristors.

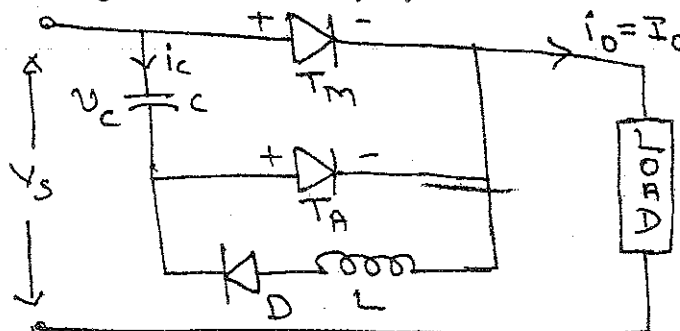


Fig. Q4(c)

(06 Marks)

PART – B

- 5 a. With the help of a neat circuit diagram and waveform, explain the operation of a bidirectional controller with 'R' load. Derive the equation for $V_{0(RMS)}$. (10 Marks)
- b. An AC voltage controller has a resistive load of $R = 10 \Omega$ and the RMS input voltage is 150 V. The thyristors are switched ON for $n = 25$ cycles and it is off for $m = 75$ cycles. Determine : i) RMS output voltage ii) Input power factor. (05 Marks)
- c. Distinguish between ON-OFF control and phase control of AC voltage controller. Which is the most widely used method? (05 Marks)
- 6 a. Explain the working of a single phase, fully controlled converter with inductive load, with the help of a neat circuit diagram and relevant waveforms. Derive the equation of V_{DC} and V_{RMS} . Assume continuous conduction. (12 Marks)
- b. A three-phase fully controlled bridge rectifier is operating from a 400 V, 50 Hz supply. The thyristors are fired at $\alpha = \frac{\pi}{4}$. There is a free wheeling diode across the load. The load current is maintained constant at 10A and the load voltage is 360 V. Compute :
i) Source inductance L_S ii) Load resistance R. (08 Marks)
- 7 a. Considering the switch to be ideal in the circuit of Fig. Q7(a), determine :
i) Duty cycle k for which the output average DC voltage and RMS voltage are equal
ii) The chopper efficiency. (04 Marks)

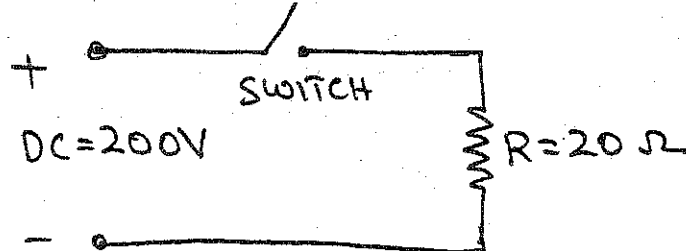


Fig. Q7(a)

- b. With a neat circuit and waveforms for continuous conduction mode, explain the working of step down chopper. (10 Marks)
- c. Draw the circuit of CLASS E four quadrant chopper and mention the devices that provide path for current in the first and third quadrant of operation. (06 Marks)
- 8 a. Briefly explain the performance parameters of an inverter. (06 Marks)
- b. What are the drawbacks of single phase half bridge inverter? Explain the operation of single phase full bridge inverter for resistive load. (08 Marks)
- c. With relevant waveforms, explain the sinusoidal pulse width modulation in an inverter. (06 Marks)
