

--	--	--	--	--	--	--	--	--	--

**Fourth Semester B.E. Degree Examination, May/June 2010**  
**Power Electronics**

Time: 3 hrs.

Max. Marks:100

*Note: Answer any FIVE full questions,  
selecting at least TWO questions from each part.*

**PART – A**

1.
  - a. What is a power electronic converter system? Draw the block diagram and mention any four applications of such a system. (06 Marks)
  - b. What is a switch? What is an ideal switch? What is a power semiconductor switch? What are the limitations of a practical semiconductor switch? (06 Marks)
  - c. What are the different power electronic converter systems? Specify the form of input and output, and mention two applications in each case. (08 Marks)
  
2.
  - a. What are the different semiconductor devices that are used as switches in power converter systems? Classify these devices based on their switching control characteristics. (06 Marks)
  - b. What is an IGBT? Draw its switching characteristics. What are its advantages over BJT and MOSFET? (06 Marks)
  - c. A power BJT is used as switch in the CE mode to connect a  $10 \Omega$  load resistance to a dc supply of 200 V. If  $V_{CE(sat)} = 2.5 \text{ V}$ ;  $V_{BE(sat)} = 1.75 \text{ V}$  and  $\beta$  of the transistor is varied from 10 to 60; calculate :
    - i) The value of base resistance  $R_B$  that results in the saturation with an overdrive factor of 4, when the base is connected to a supply of 10 V;
    - ii) The forced  $\beta$  ; and
    - iii) The power loss in the switch. (08 Marks)
  
3.
  - a. Why thyristors are called as half controlled switches? What are the modes of operation; on-state and off state conditions of a thyristor? (06 Marks)
  - b. What are the voltage and current specifications of a thyristor? Define latching current and holding current of a thyristor. (06 Marks)
  - c. Define  $\frac{dv}{dt}$  and  $\frac{di}{dt}$  capabilities of a thyristor. How are thyristors protected against high  $\frac{dv}{dt}$  and  $\frac{di}{dt}$  values? The values of protection elements of a protection circuit for a thyristor, used as a switch connecting a load to a supply are,  $R_s = 15 \Omega$ ,  $C_s = 0.1 \mu\text{F}$  and  $L_s = 150 \mu\text{H}$ . If the supply voltage is 300 V AC and load resistance is  $10 \Omega$ , calculate the maximum permissible  $\frac{dv}{dt}$  and  $\frac{di}{dt}$  values. (08 Marks)
  
4.
  - a. Define commutation of a thyristor. What are the conditions for the successful commutation? Classify the different methods of commutation. (06 Marks)
  - b. With necessary circuit diagram and wave diagrams, explain the impulse commutation technique. (06 Marks)
  - c. A load of  $40 \Omega$  is connected to a dc supply of 100V through a thyristor switch. The total inductance in the line is 0.1 H. Find the minimum width of the gate pulse required to properly turn-on the switch, if the latching current is 4mA. If the holding is 3mA with  $I_G = 0$ , what is the supply voltage below which the switch will turn-off? Take conduction drop of the thyristor as 0.8 V. (08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

## PART – B

- 5 a. Differentiate between on-off control and phase control. Define the duty cycle and delay angle in an AC voltage controller. (06 Marks)
- b. Draw the relevant circuit diagram and wave diagrams of a 1-phase full wave AC controller feeding an R-L load. What are conduction angle and extinction angle? (06 Marks)
- c. A single phase full wave AC voltage controller, using two thyristors in anti-parallel, supply a pure resistive load of  $10 \Omega$ . The input voltage is 200 V, 50 Hz. If the controller is operated at a delay angle of  $90^\circ$ , determine:
- The rms output voltage
  - The input power factor; and
  - The average and rms thyristor currents. (08 Marks)
- 6 a. Explain with circuit diagrams the differences between semi-controlled and full controlled 1-phase rectifier converter systems. (06 Marks)
- b. Draw the relevant circuit diagram and wave diagrams of a 3-phase full controlled rectifier system, supplying a pure resistive load. Explain the gating signal sequence to be used in such systems. (06 Marks)
- c. A 1-phase half wave controlled rectifier supplies a purely resistive load of  $1 \Omega$  from a 230 V, 50 Hz supply. If the average output voltage is 50% of the maximum possible value of the DC output voltage, determine:
- Delay angle of thyristors
  - RMS and average value of output current and
  - The input power factor. (08 Marks)
- 7 a. What is a chopper? How are choppers classified? Give the quadrants of operation and one application of each type. (06 Marks)
- b. Explain the basic principle operation of a step-down chopper, with necessary circuit diagram and waveforms. (06 Marks)
- c. A 15 HP, 400 V, separately excited DC motor is fed from a chopper. The input to the chopper is 440 V and the chopper operates at a duty cycle of 65%. The motor parameters are:  $R_a = 0.20 \Omega$ , Back emf constant  $K_v = 1.47 \text{ V/A-rad/sec}$ ; Motor current  $I_a = 40 \text{ A}$ ; Field current  $I_f = 1.2 \text{ A}$ . Determine:
- The power output of the chopper (which is input power to the motor)
  - The speed of the motor. (08 Marks)
- 8 a. What are the parameters that indicate the quality of an inverter? Define all of them. (06 Marks)
- b. Explain the operation of a 1-phase half bridge inverter supplying a resistive load. (06 Marks)
- c. Explain the operation of a 1-phase full bridge inverter supplying a resistive load. Derive expressions for the output RMS voltage. (08 Marks)

\* \* \* \* \*