

| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|

Sixth Semester B.E. Degree Examination, May/June 2010
Power System Analysis and Stability

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions, selecting at least TWO questions from each part.

PART - A

1. a. What is per unit quantity? Mention the advantages of per unit quantities. (06 Marks)
- b. Show that per unit reactance of two winding transformer will remain same referred to primary as well as secondary. (06 Marks)
- c. Draw the per unit reactance diagram for the power system shown in Fig. Q1(c).

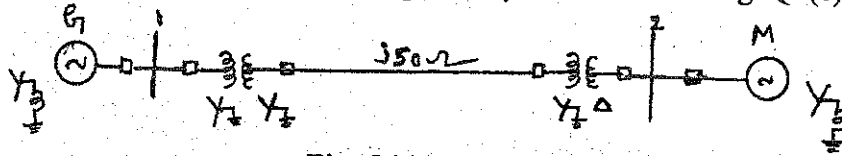


Fig. Q1(c)

The rating of the generator, motor and transformers are:
 Generator : 40 MVA, 25 KV, $X'' = 20\%$
 Motor : 50 MVA, 11KVA, $X'' = 30\%$
 Y-Y transformer : 40 MVA, 33Y/220YKV, $x = 15\%$
 Y- Δ transformer : 30 MVA, 11 Δ /220YKV, $X = 15\%$
 Use a base of 100 MVA, 220 KV in 50 Ω line.

(08 Marks)

2. a. Determine Y_{BUS} by inspection method for the system details given in Table.1 (06 Marks)

| | | | | | |
|------------------------------|-------|-------|-------|-------|-------|
| Bus code | 1 - 2 | 2 - 4 | 3 - 4 | 3 - 1 | 1 - 4 |
| Series reactance of the line | j0.20 | j0.25 | j0.15 | j0.10 | j0.30 |

Table.1

- b. Explain clearly, how circuit breakers are rated? (06 Marks)
- c. A generator is connected to a synchronous motor through transformer. Reduced to a common base, the per unit sub transient reactances of generator and motor are 0.15 and 0.35 pu respectively. The leakage reactance of the transformer is 0.1 pu. A 3 ϕ short circuit fault occurs at terminals of the motor when terminal voltage of generator is 0.9 pu and output current of the generator is 1 pu at 0.8 pf leading. Find the sub transient current in the fault, generator and motor. (08 Marks)

3. a. What are symmetrical components? How they are useful in solution of power system. (04 Marks)
- b. Derive an expression for the 3 ϕ complex power in terms of symmetrical components. (08 Marks)
- c. A delta connected balanced resistive load is connected across a balanced 3 ϕ supply as shown in Fig.Q3(c), with currents in lines A and B specified. Find the symmetrical components of the currents. (08 Marks)

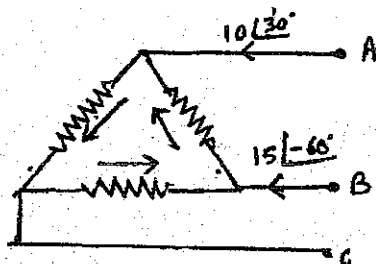


Fig.Q3(c)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

- 4 a. With the help of relevant vector diagrams for voltages and currents, establish the phase shift of symmetrical components in Y - Δ transformer. (12 Marks)
- b. What are sequence impedances and sequence networks? Draw the zero sequence networks for different combinations of 3 ϕ transformer bank. (08 Marks)

PART - B

- 5 a. What are the different types of faults occurring in electrical power system and probability of occurrence? List out in the ascending order of their severity. (04 Marks)
- b. A double line to ground fault occurs at the terminals of an unloaded generator. Derive an expression for the fault currents. Also draw connection of sequence networks. (10 Marks)
- c. Discuss briefly the open-conductor faults in power system. (06 Marks)
- 6 A single-line to ground fault occurs at mid point F of transmission line in power system shown in Fig.Q6. Determine the fault current in pu and in amperes from the generator if the system were on no load and at a voltage of 100 KV at the fault point.

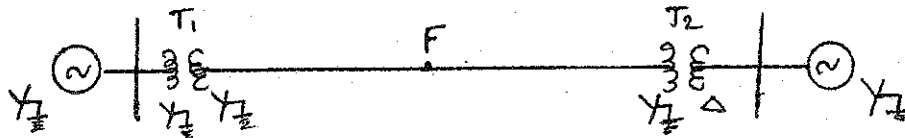


Fig.Q6

The ratings are:

Generator : 11.5 KV, 50 MVA, $X_1 = 0.3$ pu, $X_2 = 0.2$ pu, $X_0 = 0.1$ pu

Motor : 6 KV, 55 MVA, $X_1 = 0.4$ pu, $X_2 = 0.3$ pu, $X_0 = 0.2$ pu

Line : $X_1 = X_2 = 48.5 \Omega$, $X_0 = 90 \Omega$

Transformer - T_1 : 11/110 KV, 45 MVA, $X = 0.1$ pu

Transformer - T_2 : Consists of three single phase units each rated 20 MVA, 66 KV/6.6 KV, $X = 10\%$.

Use base of 60 MVA, 110 KV in transmission line. (20 Marks)

- 7 a. Differentiate between steady state and transient state stability of a power system. Can these stability limits have multiple values? (06 Marks)
- b. Derive the power angle equation of salient pole m/c connected to infinite bus. (06 Marks)
- c. Derive swing equation with usual notation. (08 Marks)
- 8 a. Briefly explain the methods of improving steady state and transient state stability of a power system. (04 Marks)
- b. Explain the equal area criterion for investigating the stability of power system. (08 Marks)
- c. An ac generator is delivering 50% of maximum power to an infinite bus. Due to a sudden short circuit, the reactance between generator and infinite bus increases to 500% of the value before fault. The maximum power that can be delivered after clearance of the fault is 75% of the original value. Calculate the critical clearing angle to maintain the stability of the system. (08 Marks)
