

USN

--	--	--	--	--	--	--	--

EC64

Sixth Semester B.E. Degree Examination, December 2010

Digital System Design using VHDL

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions.

- 1 a. Distinguish between variables and signals. Give examples. (04 Marks)
- b. Write VHDL models for a 4-to-1 multiplexer. (08 Marks)
- c. Write VHDL structural model for the circuit shown in fig. Q1 (c). (08 Marks)

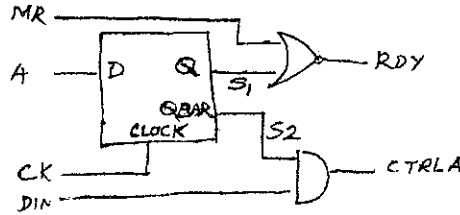


Fig. Q1 (c)

- 2 a. Discuss general model of mealy sequential machine. How do you realize mealy sequential network with a ROM? (08 Marks)
- b. What is programmable logic array? Give suitable example. (08 Marks)
- c. Explain assert statement and report statement. Give examples. (04 Marks)
- 3 a. Design a binary multiplier and hence write VHDL code (behavior model) for 4×4 binary multiplier. (10 Marks)
- b. Write a block diagram for signed divider with state graph for signed divider control network and write test bench for signed divider. (10 Marks)
- 4 a. With the help of case construct, write VHDL code for SM chart for binary multiplier. (07 Marks)
- b. Describe alternative realizations for SM charts using microprogramming. (07 Marks)
- c. Write a note on linked state machines. (06 Marks)
- 5 a. Mention the steps to be followed, when designing with FPGAS, a digital system. (08 Marks)
- b. Describe input output block-Xilinx 3000 series. (04 Marks)
- c. Discuss the features of Altera complex programmable logic devices (CPLDS). (08 Marks)
- 6 a. Explain multivalued logic and signal resolution with examples. (08 Marks)
- b. Distinguish between inertial delay and transport delay. (04 Marks)
- c. Describe synthesis of VHDL code with examples. (08 Marks)
- 7 a. Explain STATIC RAM memory. Write simple memory model in VHDL. (10 Marks)
- b. Explain how 486 bus interface is done to a memory system and hence draw SM chart for simplified 486 bus interface. (10 Marks)
- 8 Write short notes on the following:
 - a. FPGA and CPLD.
 - b. Generics.
 - c. Operator overloading.
 - d. Package.(20 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

