

Seventh Semester B.E. Degree Examination, December 2010
VLSI Circuits and Design

Time: 3 hrs.

Max. Marks:100

Note: 1. Answer any FIVE full questions, selecting at least TWO questions from each part.
2. Any missing data may be assumed suitably.

PART - A

- 1 a. With neat diagrams, explain the working of enhancement mode NMOS transistor, for different values of V_{DS} . (08 Marks)
 b. What are the advantages if N-well CMOS circuits? List the main steps involved in N-well CMOS fabrication. (06 Marks)
 c. Draw the structure of a P-well CMOS inverter. Neatly label the parts. (06 Marks)
- 2 a. Show that pull-up to pull-down ratio for an NMOS inverter, driven through one or more pass transistors, is 8:1. (10 Marks)
 b. With neat circuit diagrams, explain the merits and demerits of BiCMOS inverter configurations. (10 Marks)
- 3 a. Draw the stick diagram and layout for an NMOS two way selector, with enable input. (06 Marks)
 b. What are design rules? Give the significance of lambda based design rules. With neat diagrams, explain lambda based design rules as applicable to MOS layers and transistors. (08 Marks)
 c. What are the advantages of a complementary transistor pull-up, for an inverter? With relevant diagrams, explain the CMOS inverter operation in different regions. (06 Marks)
- 4 a. Calculate the resistance between V_{DD} and V_{SS} of an NMOS inverter with pull - up to pull - down ratio = 4 and show that the ratio rule does not apply for CMOS inverter. Take lambda = 5 μm . (06 Marks)
 b. Calculate the total capacitance in pico farads between the substrate and the structure shown in Fig.Q.4(b) for lambda = 5 μm . Use standard values. (08 Marks)

 


Fig.Q.4(b).

- c. Give the concept of sheet resistance, square capacitance and delay unit. (06 Marks)

PART – B

- 5 a. Explain different scaling models by considering the relevant diagram of an NMOS transistor. (06 Marks)
- b. Obtain the scaling factors for the following transistor parameters, by considering the constant voltage scaling model :
- i) Gate area
 - ii) Gate capacitance per unit area
 - iii) Gate capacitance. (06 Marks)
- c. By considering a suitable example, compare the metal interconnect and electro – optical interconnect models. (08 Marks)
- 6 a. Explain the structured design approach for an n – bit bus arbitration logic and draw the NMOS stick diagram for its basic cell. (10 Marks)
- b. With a suitable example, explain the concept of dynamic CMOS logic. (10 Marks)
- 7 a. What is two phase clocking? Draw and explain a combinational circuit to generate a two phase clock. (06 Marks)
- b. With a neat diagram and relevant expressions, explain the implementation of a 4 bit ALU, using full adders. (12 Marks)
- c. What is regularity? Explain. (02 Marks)
- 8 Write short notes on :
- a. Super buffers.
 - b. Barrel shifter.
 - c. Switch logic. (20 Marks)
 - d. Dynamic shift register.
