

--	--	--	--	--	--	--	--	--	--

Sixth Semester B.E. Degree Examination, December 2010
Electronic Instrumentation

Time: 3 hrs.

Max. Marks:100

**Note: Answer any FIVE full questions, selecting
at least TWO questions from each part.**

PART – A

- 1
 - a. State the three types of systematic errors giving examples for each. (06 Marks)
 - b. The current through a resistor is 2.5 A, but the measurement yields a value of 2.45 A. Calculate the absolute error, percentage error, relative accuracy and percentage accuracy. (04 Marks)
 - c. How is voltage in microvolts range measured? Explain with the help of a neat diagram. What is the use of chopper in micro voltmeter? (10 Marks)
- 2
 - a. Differentiate between shunt type and series type ohm meter. (04 Marks)
 - b. A series ohm meter uses a 50Ω basic measurement requiring a full scale deflection of 1 mA. The internal battery voltage is 3 V. The desired scale marking for half scale deflection is 2000Ω . Calculate :
 - i) Values of R_1 and R_2
 - ii) Maximum value of R_2 to compensate 10% drop in battery. (06 Marks)
 - c. Explain with the help of a neat circuit diagram, the working of dual slope DVM. (08 Marks)
 - d. An integrator contains $100 K\Omega$ and $1 \mu f$ capacitor. If the applied voltage to the integrator input is 1 V, what voltage will be present at the output of integrator after 1 sec? (02 Marks)
- 3
 - a. Explain the operation of digital multimeter. (07 Marks)
 - b. Explain with the help of a neat sketch, the working of digital frequency meter. (06 Marks)
 - c. Explain the operation of digital capacitance meter. (07 Marks)
- 4
 - a. List specifications that should be considered while selecting a recording instrument. (04 Marks)
 - b. Explain the working of X – Y recorder. (06 Marks)
 - c. Describe applications of recording instruments. (04 Marks)
 - d. Explain the working of strip chart recorder. (06 Marks)

PART – B

- 5
 - a. Draw a block diagram of a function generator. Explain the method of producing sine waves. (10 Marks)
 - b. Mention standard specifications of signal generator. (04 Marks)
 - c. List the various controls on the front panel of a pulse generator. Mention their uses. (06 Marks)
- 6
 - a. Explain with the help of a neat diagram, the working of vector impedance meter. (08 Marks)
 - b. How is field strength measured? (06 Marks)
 - c. How can a Q-meter be used for the measurement of:
 - i) D.C resistance of a circuit
 - ii) Stray capacitance. (06 Marks)

- 7 a. On what principle does R-X meter operate? Explain. (06 Marks)
b. How can transistor tester be used for measurement of the following?
i) Faulty transistor
ii) Beta gain (06 Marks)
c. What are the functions of transducer? (04 Marks)
d. List four types of electrical pressure transducer. Describe the application of each type. (04 Marks)
- 8 a. Explain the operating principle of LVDT. (06 Marks)
b. Explain seven segment LED display. (04 Marks)
c. What are the advantages of LCD display over Nixie tube and LED display? (04 Marks)
d. What are the operating principles of LCD display? (06 Marks)

* * * * *