

Fifth Semester B.E. Degree Examination, December 2010
Fundamentals of CMOS VLSI

Time: 3 hrs.


Max. Marks:100

Note:1. Answer any FIVE full questions, selecting atleast TWO questions from each of Part - A and Part - B.
2. Missing data may be assumed suitably.

PART - A


1.
 - a. What do you mean by static load inverters? Derive the output voltage for the pseudo inverter by discussing its DC transfer characteristics. (08 Marks)
 - b. In a $0.5\mu\text{m}$ process $\mu_n = 44.69 \times 10^{-3} \text{ m}^2/\text{V}$, $t_{\text{ox}} = 14.1\text{nm}$ and the $(W/L) = \frac{30}{5}$. The NMos has $V_t = 0.71\text{V}$ and $V_{\text{gs}} = 1.5\text{V}$. At what levels of V_{ds} and i_{d} , will the MOSFET reach pinch off mode? Hint : $(\epsilon_{\text{ox}} = 3.9\epsilon_0)$. (06 Marks)
 - c. What is the functionality of the circuit shown in fig. Q1(c). Is it correct method to connect the circuit as shown in figure Q1(c)? Justify your answer. (06 Marks)

Fig. Q1(c)

 

2.
 - a. Draw the Cmos circuit for half adder. (Hint : Sum = $A \oplus B$, carry = AB , Inverted i/p's are allowed). (08 Marks)
 - b. Draw the circuit diagram for the layout diagram shown in fig. Q2(b). (08 Marks)

Fig. Q2(b)

 


3.
 - a. What are the basic layers of MOS circuit? (04 Marks)
 - b. Explain the working principle of dynamic CMOS logic and clocked CMOS logic of "Nand" gate. (12 Marks)
 - c. Implement the pass transistor logic circuit for the expression $Y = A + BC$. Show the design steps clearly. (08 Marks)
4.
 - a. Discuss the limitations of scaling. (10 Marks)
 - b. Derive the expression for total delay for N stage of NMOS and CMOS inverters by assuming the width factor $f = e$. (10 Marks)

PART - B

- 5 a. In the circuit shown in fig. Q5(a), find V_1 , V_2 , V_3 , V_4 and V_5 . Justify your answer.

(08 Marks)

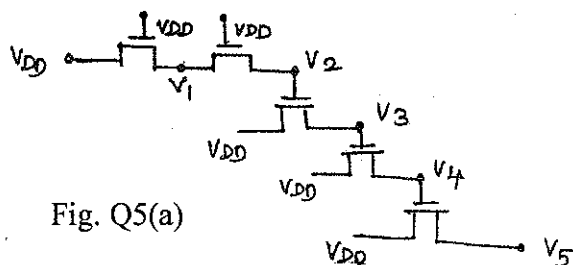

- b. Explain NMOS and CMOS non – inverting dynamic storage cell and draw the 3 – bit shift register using the CMOS dynamic storage cell. (12 Marks)
- 6 a. Draw and explain the 8 – bit carry select adder dividing it into $m = 2$ blocks. Calculate the completion time ‘T’ by assuming the one adder delay is 4ns and one mux delay is 2ns. (12 Marks)
- b. Draw the block diagram and clearly show the switch connections to perform the logic operation of “OR” and “XOR” in a 3 – bit ALU using a standard adder element. (08 Marks)
- 7 a. Explain four transistor dynamic and six transistor static memory cells. Reason out the need for sense amplifier in the cell array. (14 Marks)
- b. Explain the CMOS pseudo – static D flipflop. (06 Marks)
- 8 a. What is multiplexed D flipflop? Explain the general method for testing with scan path approach. (08 Marks)
- b. What are the three important steps in sensitized path based testing? (06 Marks)
- c. Find the test vectors to detect the stuck @ 0 and stuck @1 faults of “and” gate at its input and output node. Fig. 8(c). (06 Marks)

Fig. Q8(c)

