

Seventh Semester B.E. Degree Examination, May/June 2010
Power Electronics

Time: 3 hrs.


Max. Marks:100

Note: Answer any FIVE full questions, selecting at least TWO questions from each part.

PART - A


1. a. List out some applications of power controller. (06 Marks)
- b. Write the characteristic features of following power devices. (10 Marks)
i) SCR ; ii) TRIAC ; iii) LASCR ; iv) MCT ; v) SITH.
- c. Compare the characteristic of power MOSFET and IGBT. (04 Marks)
2. a. Discuss the steady state characteristics power MOSFETS compare this with characteristics of power BJT. (10 Marks)
- b. The beta (β) bipolar transistor shown in Fig.2(b) below varies from 12 to 75. The load resistance $R_C = 1.5 \Omega$. The dc supply voltage is $V_{CC} = 40 \text{ V}$ and input voltage to the base circuit $V_B = 6 \text{ V}$, if $V_{CE(sat)} = 1.2 \text{ V}$, $V_{BE(sat)} = 1.6 \text{ V}$, $R_B = 0.7 \Omega$. Determine : (10 Marks)
i) Overdrive factor (ODF)
ii) The forced β and
iii) The power loss in the transistor P_T .

Fig.2(b)

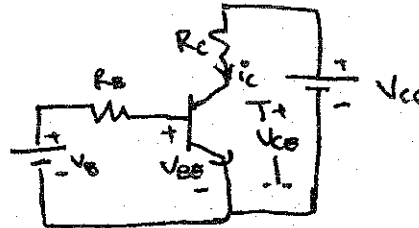

3. a. Define the following term with respect to SCR : (08 Marks)
i) Latching current ; ii) Holding current
iii) Turn-on time ; iv) Turn off time.
- b. The latching current for SCR inserted in between a dc voltage source of 200 V and load is 100 mA. Calculate the minimum width gate pulse current required to turn-on this SCR in case the load consist of i) $L = 0.2 \text{ H}$; ii) $R = 20 \Omega$ in series with $L = 0.2 \text{ H}$. (06 Marks)
- c. With help of neat circuit diagram and waveforms, explain RC firing circuit used with half controlled rectifier. (06 Marks)
4. a. What is the need of di/dt protection and dv/dt protection? Explain how protection is provided. (04 Marks)
- b. The input voltage of Fig.4(b), $V_s = 200 \text{ V}$ with load resistance $R = 5 \Omega$ and the load and stray inductance are negligible and thyristor is operated at $f_s = 2 \text{ kHz}$. If the required dv/dt is $100 \text{ V}/\mu\text{s}$. The discharge current is limited to 100 A. Determine : (08 Marks)
i) The values R_s and C_s ; ii) The snubber loss.

Fig.4(b)

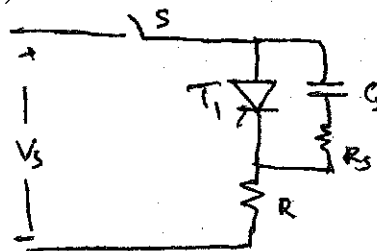

- c. Explain the operation of single phase semi-converter with highly inductive load. Derive the expression for V_{dc} and V_{rms} . (08 Marks)

PART - B

- 5 a. What is forced commutation? With help of neat diagram and relevant equations, explain the operations of self commutation circuit. (10 Marks)
- b. Derive the equation for turn-off time of SCR in impulse commutated circuit for the following circuit. For the impulse commutated thyristor circuit shown in Fig.5(b). Determine turn-off time of the circuit for $R = 10 \Omega$ and $C = 20 \mu F$ and supply voltage $V_s = 220 V$. (10 Marks)

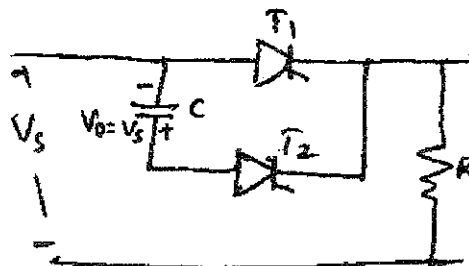


Fig.5(b)

- 6 a. What are advantages and disadvantages ON-OFF control and phase control of ac voltage controller? (08 Marks)
- b. For the AC voltage controller shown in the following fig.6(b), the delay angles of thyristors are equal and $\alpha_1 = \alpha_2 = \frac{2\pi}{3}$. Determine the :
 i) RMS O/P voltage
 ii) Input power factor
 iii) Average and Rms current of the thyristors.

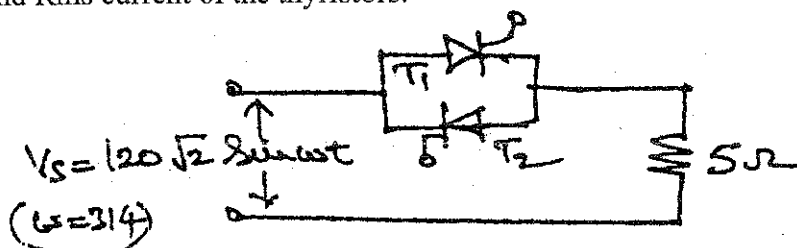


Fig.6(b)

- 7 a. What is chopper? Explain principle of step up chopper with relevant equations. (10 Marks)
- b. Give the classification of chopper. Explain briefly each one of them. (10 Marks)
- 8 a. Write the principle of operation of 1 - ϕ inverter with relevant diagram and waveform. Also discuss the performance parameter. (10 Marks)
- b. The 1 - ϕ full bridge inverter has resistive load $R = 2.4 \Omega$ the dc input voltage $V_s = 48 V$. Determine :
 i) RMS output voltage at fundamental frequency
 ii) The output power
 iii) The average and peak current of each transistor. (10 Marks)
